




UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386



MuPix9 - a HV-MAPS prototype with serial powering

Alena Weber, Heiko Augustin, Ivan Peric, Mridula Prathapan

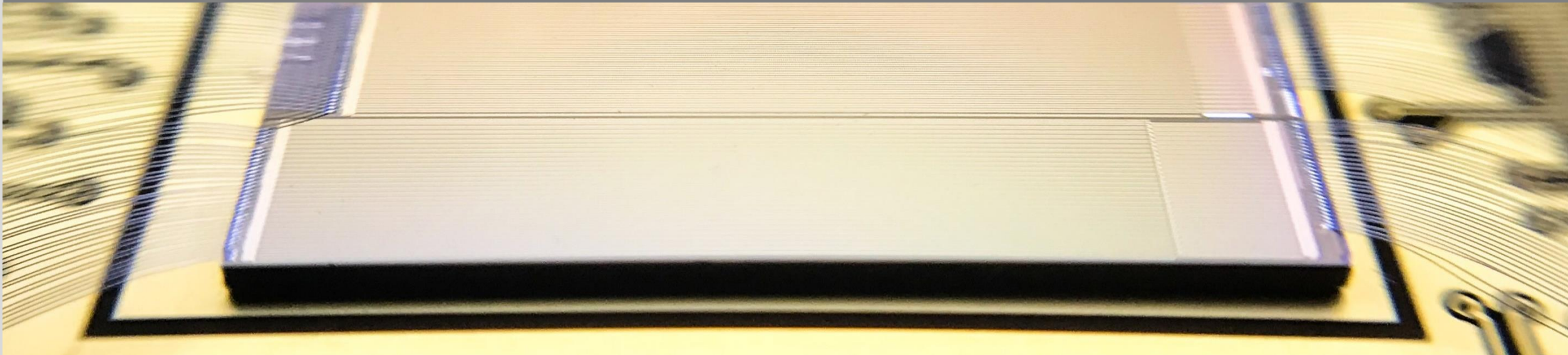ASIC and Detector Laboratory, Karlsruhe Institute of Technology and University Heidelberg




Outline



- Overview of the MuPix9
- Regulator element
- Serial powering – Introduction to standard concepts
- Serial powering – Introduction to HVCMOS concepts
- Chip interconnection concepts for serial powering
 - Concept 1: vdda and vssa separated
 - Concept 2: vdda = vssa
 - Concept 3: shared voltage
 - Concept 4: analog part serial and digital part parallel
- Version implemented on MuPix9
- Vision for next generation MuPix
- Outlook

Overview of the MuPix9


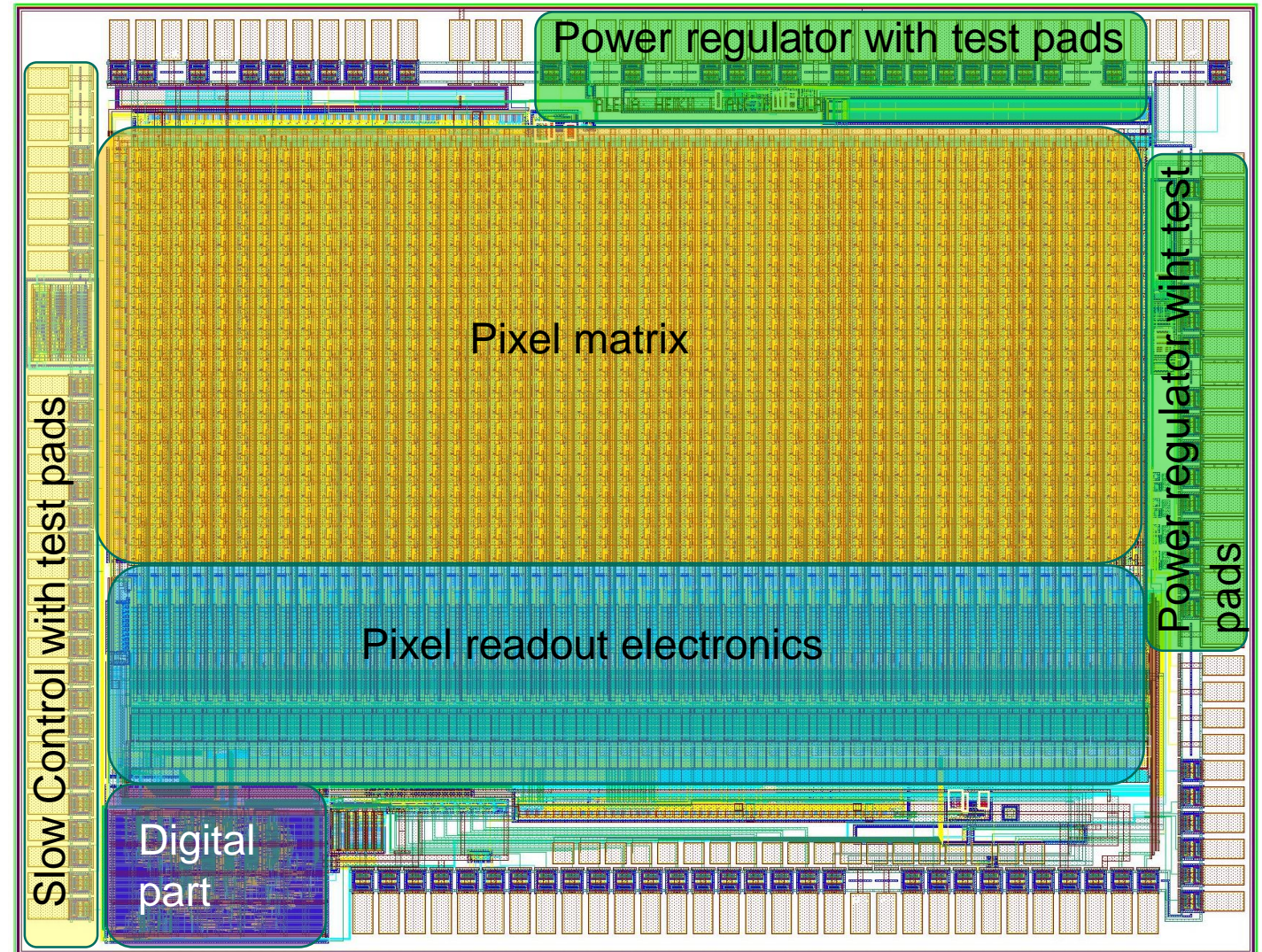
- Small sensor prototype (4700 μm x 3600 μm)
- AMS aH18 HV-CMOS
 - Minimal gate length of 180nm
 - Substrate with 20 Ωcm
 - 48 columns each with 20 pixels
- Main parts:
 - Pixel matrix
 - Pixel readout electronics
 - Digital part with slow control
 - Slow control as stand-alone part
 - Two power regulators



Overview of the MuPix9



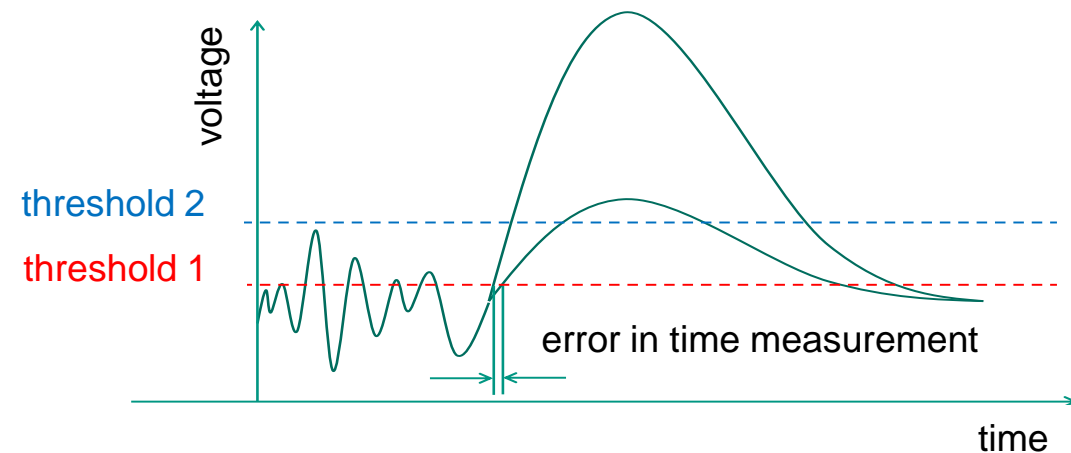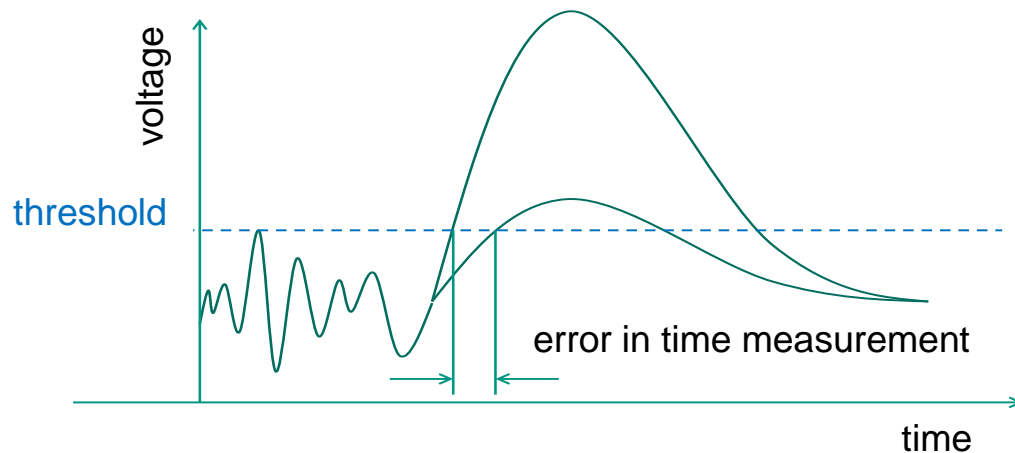- Changes in comparison to MuPix8
 - one pixel matrix
 - Pixels in NMOS instead of PMOS
 - Readout cells are modified: now with capacitor for capacitive coupling for serial powering. Three modes concept from MuPix8 is kept.




- Digital part with modified state machine and new slow control
- slow control as stand-alone part

Regulator Element



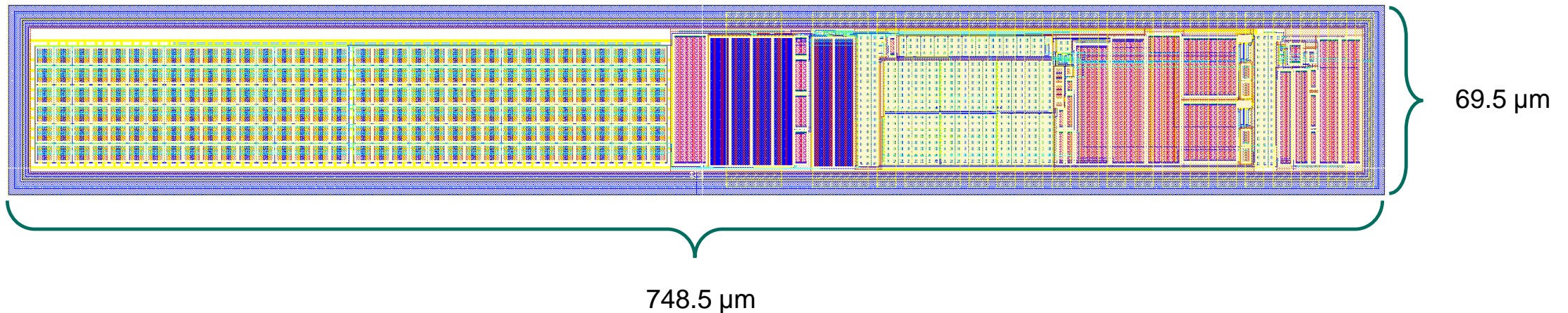
- Same element with very small modifications for every solution
- Very small temperature dependency
- 8 tune bits
- Actual design as simple as possible, without linear regulator and as less space consuming as possible



Regulator Element



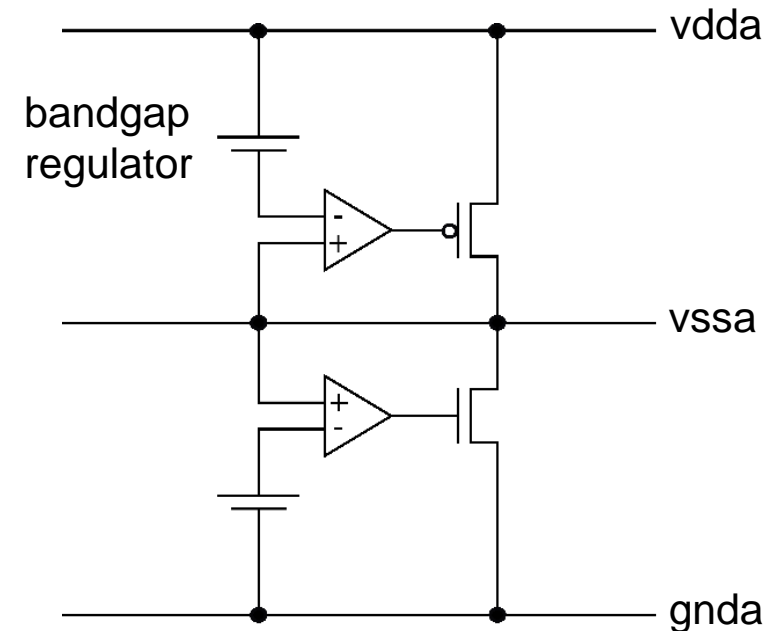- Same element with very small modifications for every solution
- Very small temperature dependency
- 8 tune bits
- Actual design as simple as possible, without linear regulator and very compact
- Functional concept is shown here:
 - bandgap regulator works like a battery, which supply a fixed current
 - in real circuit only one bandgap, current is mirrored
 - two differential amplifiers




Serial powering – Introduction to standard concepts



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386




■ Parallel Powering

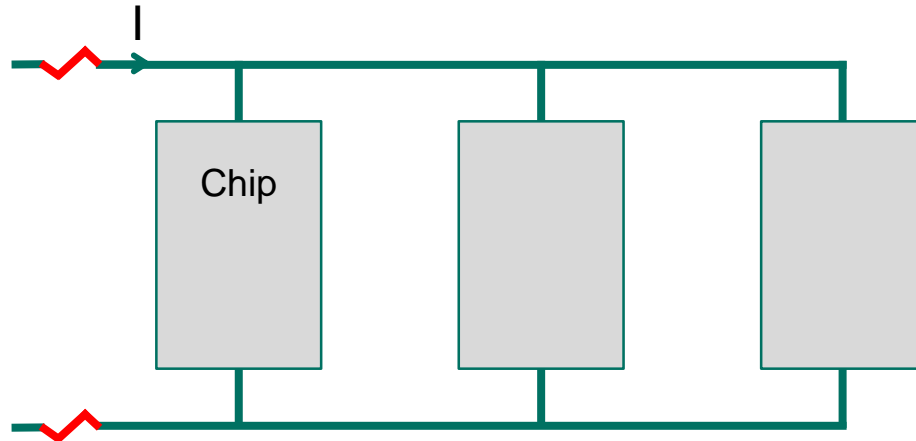

- chip connection parallel, all outputs on same voltage level

■ Serial Powering

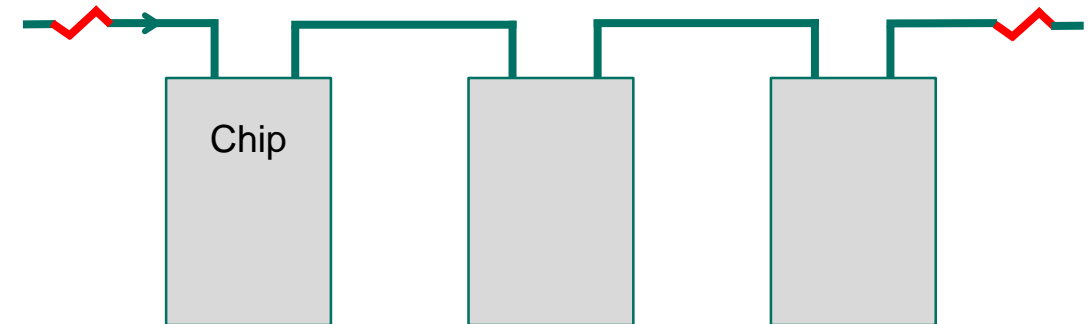

- chip connection serial, all outputs on a different voltage level


Serial powering – Introduction to HVCMOS concepts



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386




■ Parallel Powering

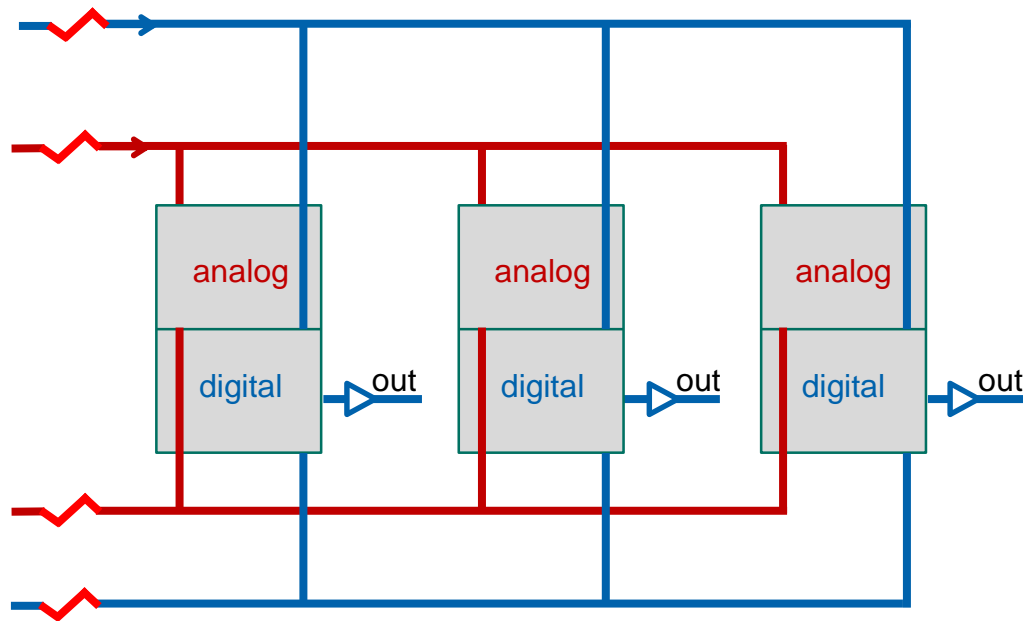

- Analog and digital powering separated in two circuits
- All digital levels are the same

■ Serial Powering

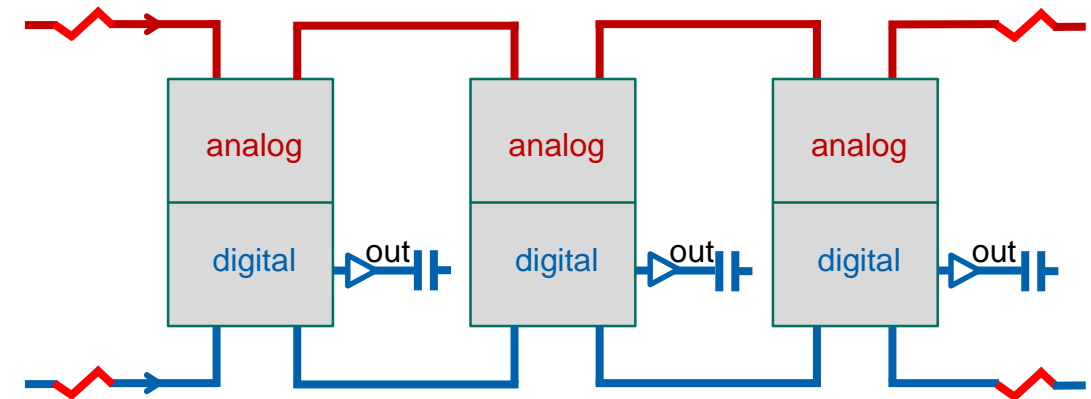


- chip connection serial, all outputs on a different voltage level
- Solution: conductive coupling

Chip interconnection concepts for serial powering

Concept 1: vdda and vssa separated

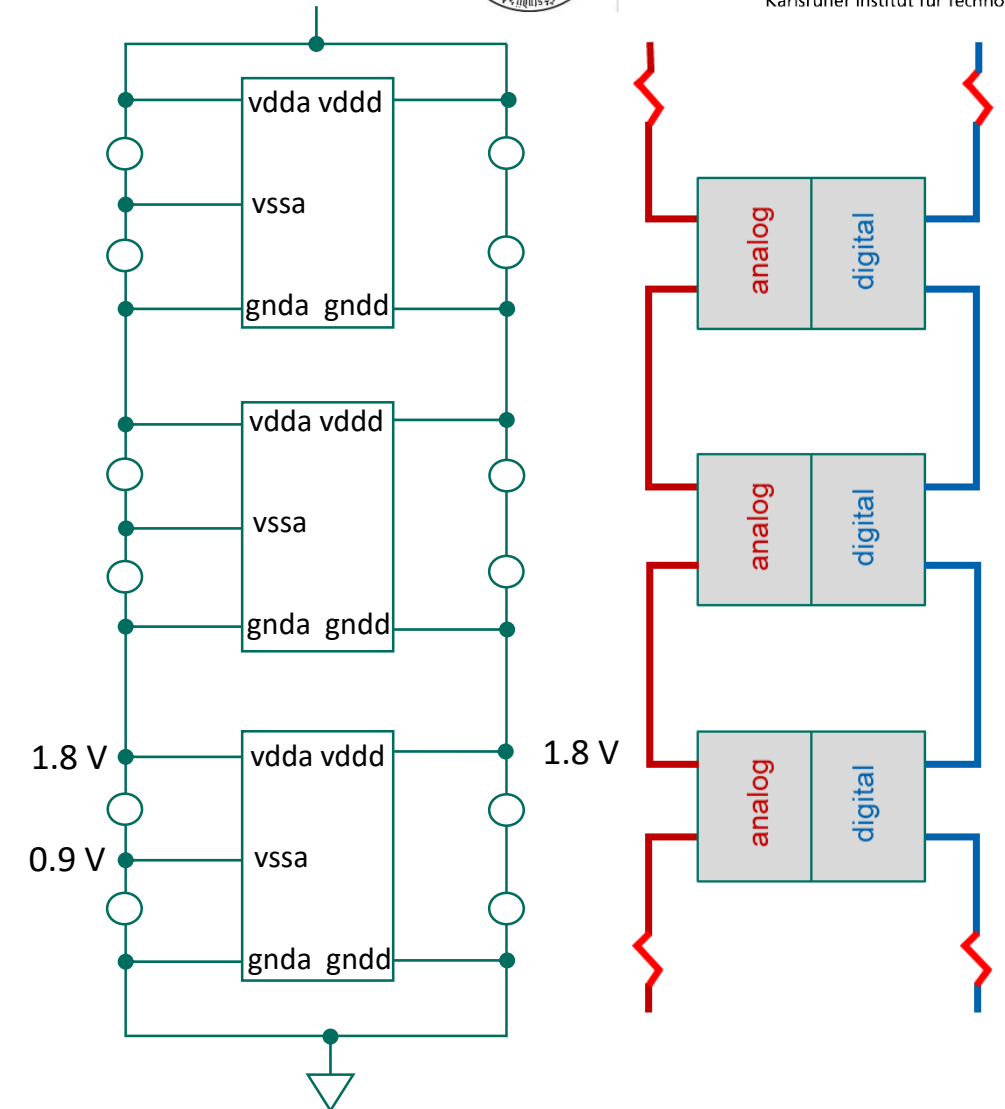
- Analog and digital voltage separated for lower noise
- Analog part with vdda (1.8 V) and vssa (0.9 V)
- Regulator element represented with two circles



Chip interconnection concepts for serial powering

Concept 2: $v_{dda} = v_{ssa}$

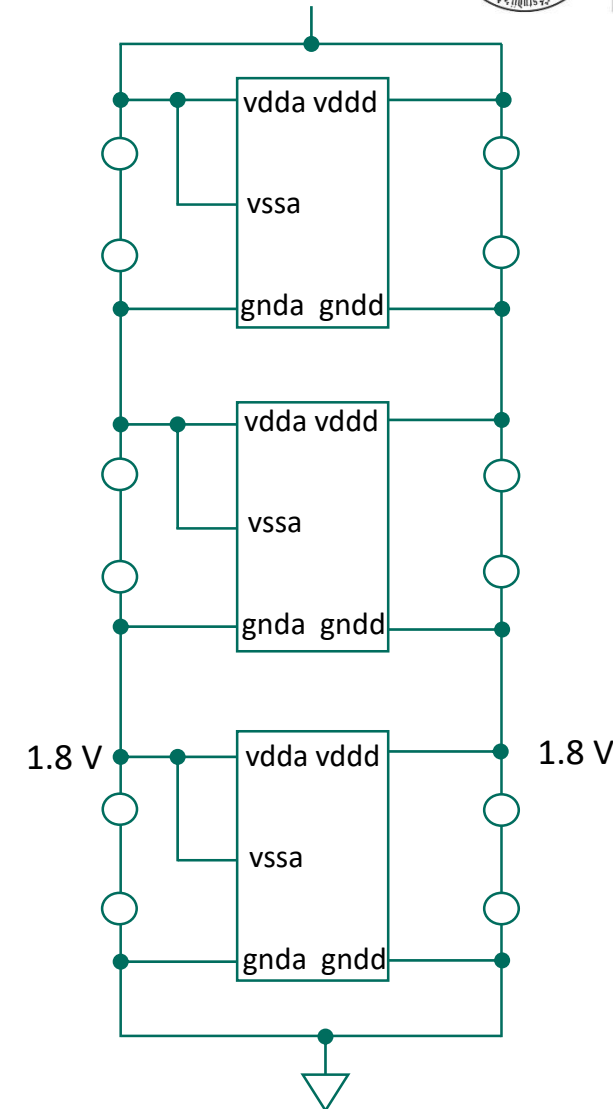
- Similar to concept 2, but:
- $v_{ssa} = v_{dda} = 1.8 \text{ V}$
- Redesign of pixel amplifier necessary



Chip interconnection concepts for serial powering

Concept 3: shared voltage

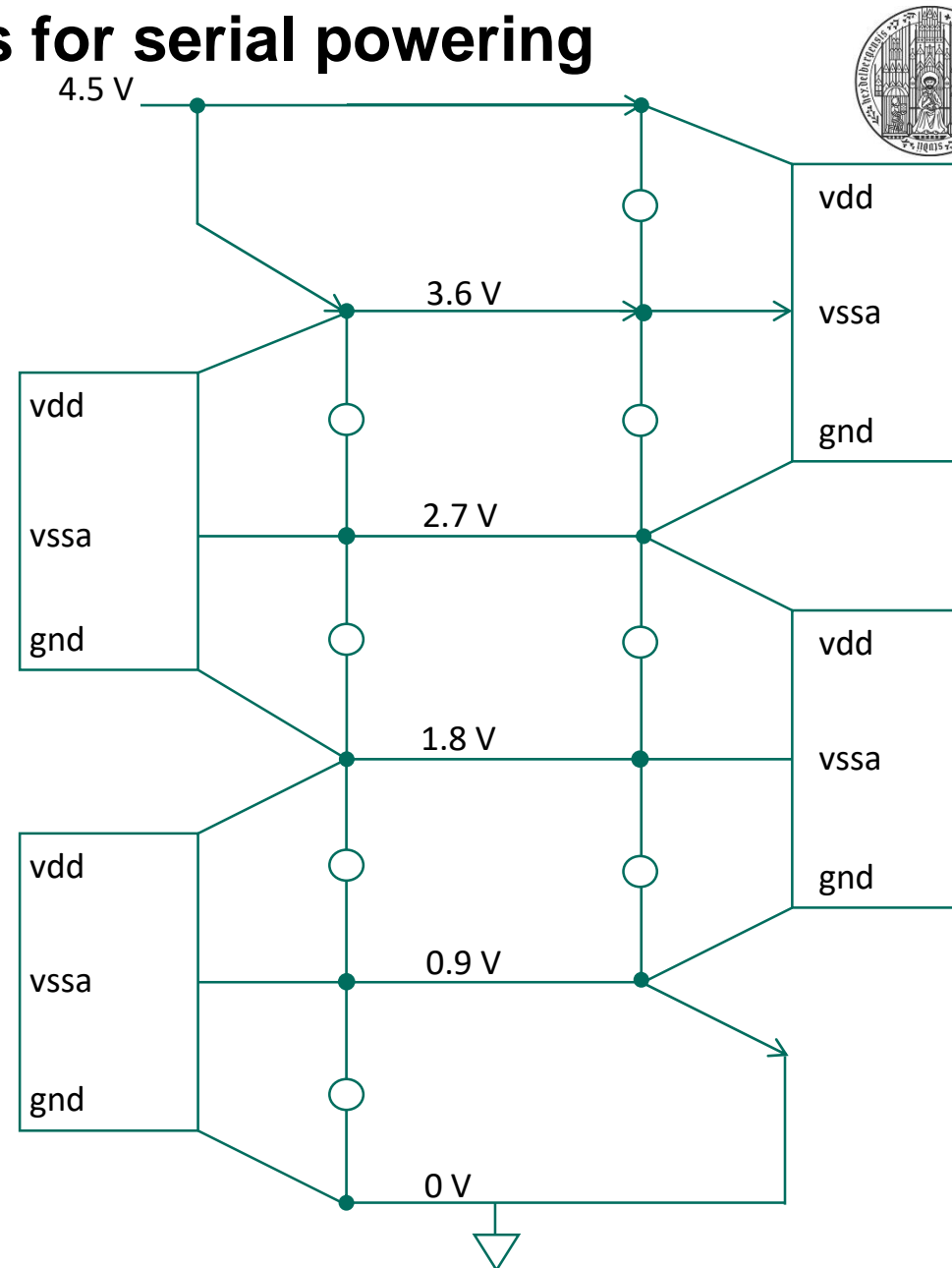
- Lower input current
- Less power consumption
- “Shared voltage”



Chip interconnection concepts for serial powering

Concept 3: shared voltage

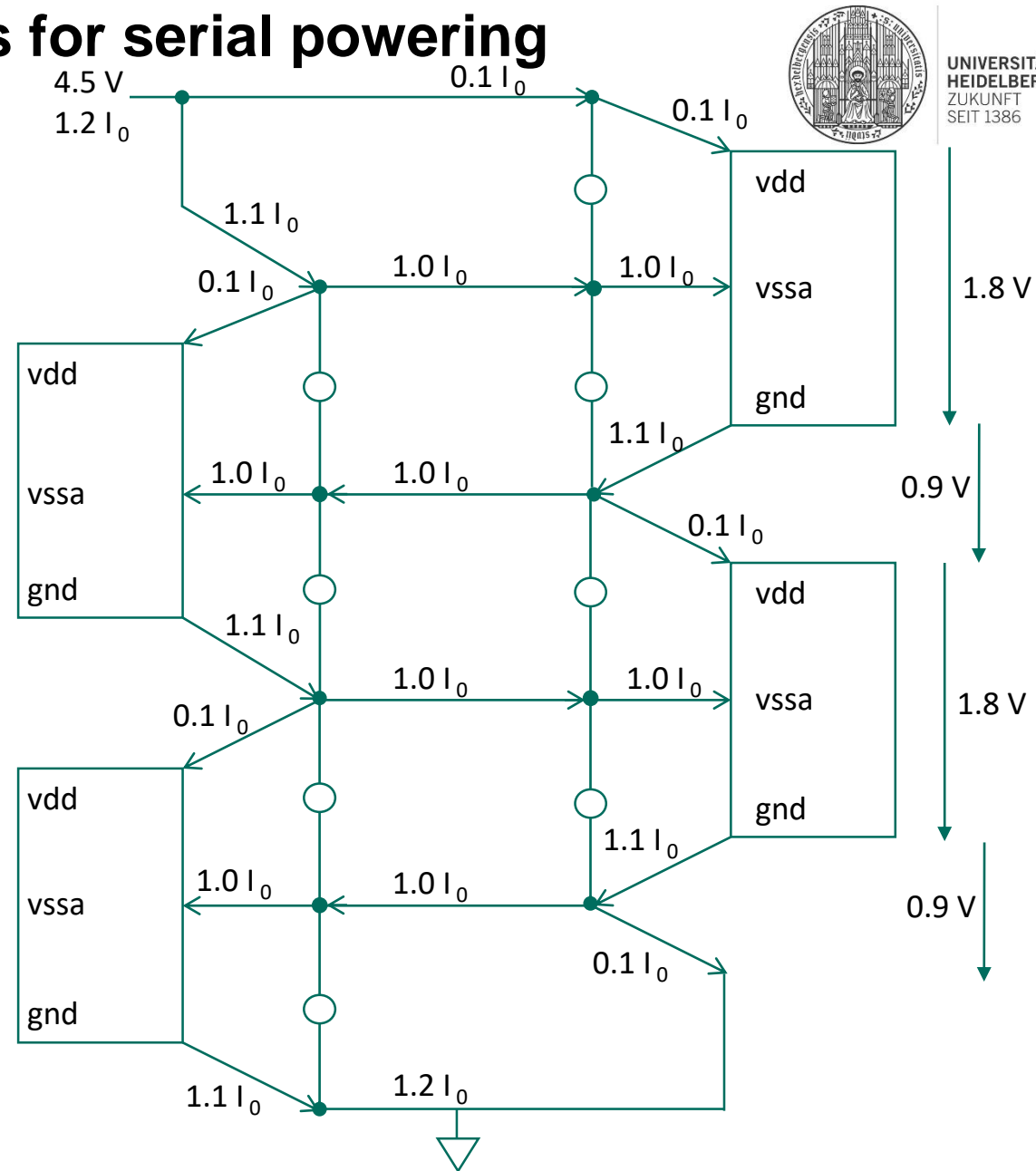- Lower input current
- Less power consumption
- “Shared voltage”



UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386




Chip interconnection concepts for serial powering

Concept 4: analog part serial, digital part parallel



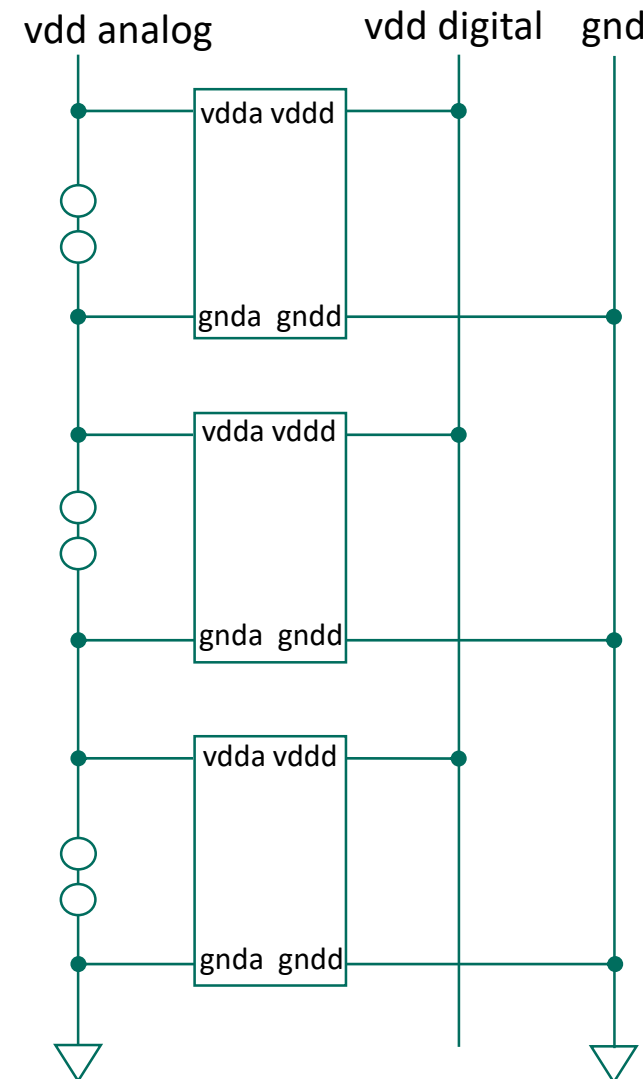
- Analog and digital voltage separated
- Analog part serial, digital part parallel
- For analog part all concepts that were presented can be used



Version implemented on MuPix9



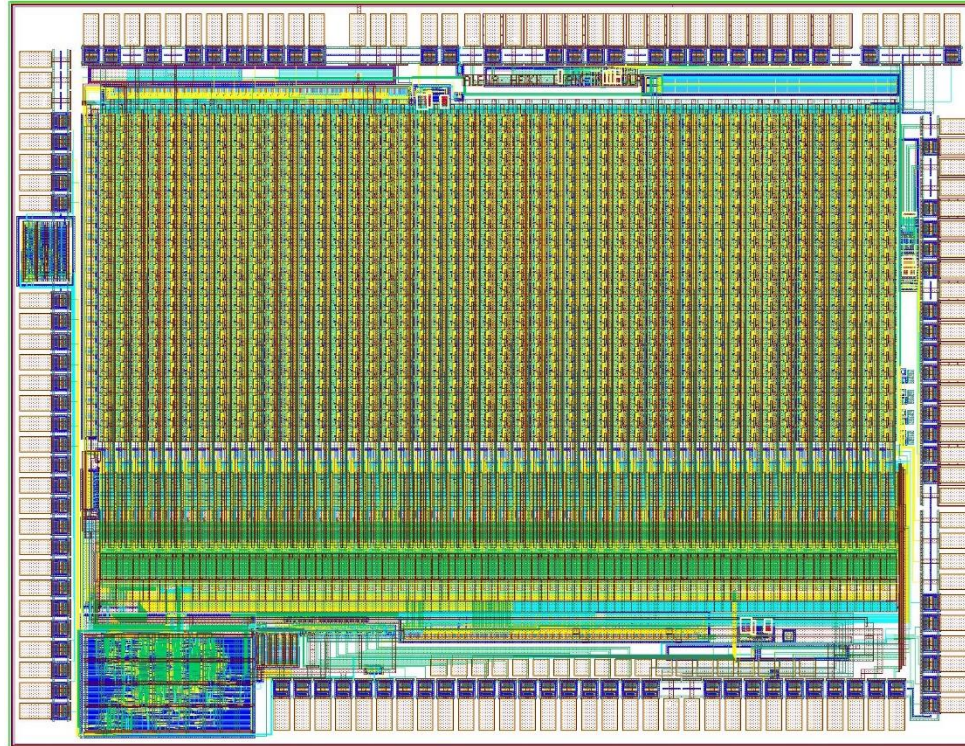- Analog and digital power separated and capacitive coupled
- Two power regulators, one for the analogue part and one for the digital part
- Each power regulator can be tested as stand alone without out the matrix but also can be connected to the pixel matrix



Vision for next generation MuPix




UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386


KIT
Karlsruher Institut für Technologie

- On a full-size MuPix: three submatrices similar to MuPix8, but every submatrix identical
 - submatrices powered in serial
 - digital and analog power disconnected and captive coupled
 - chips powered in parallel
 - leads to a current reduction of 2/3

3 submatrices
parallel powered

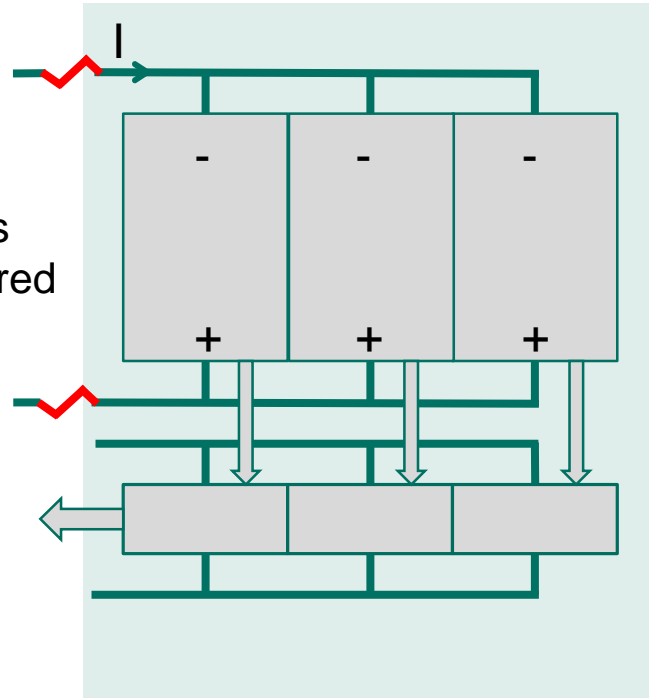

3 submatrices
serial powered

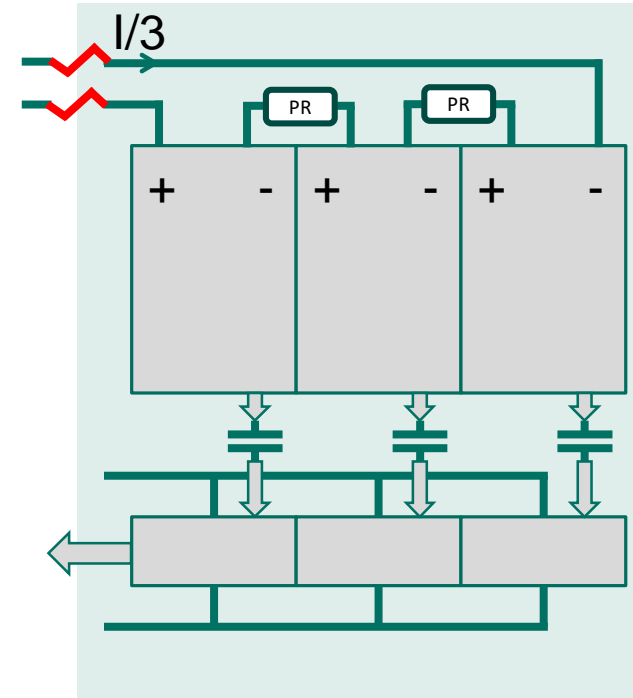

Outlook

- In summer 2018 start testing of MuPix9
- Based on the test results of MuPix9 further improvement of the design of the power regulator
- With results review of the serial power concepts and decision for one solution
- Next submission maybe end of 2018
- Final MuPix release in 2019
 - Minimal number of pads at the bottom side
 - Divided pixel matrix
 - Small pixel readout electronics
 - State machine with slow control
 - Two power regulators

